
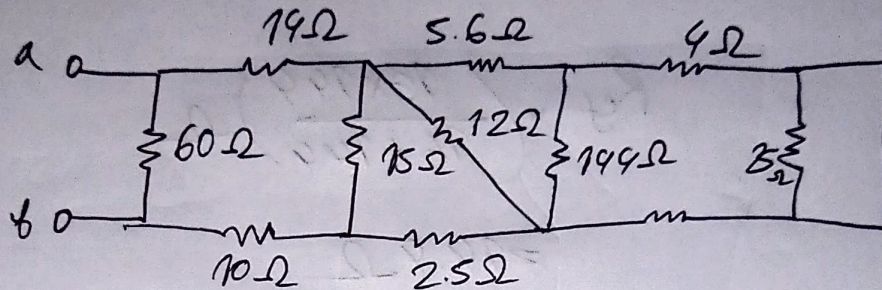


## Assignment-1

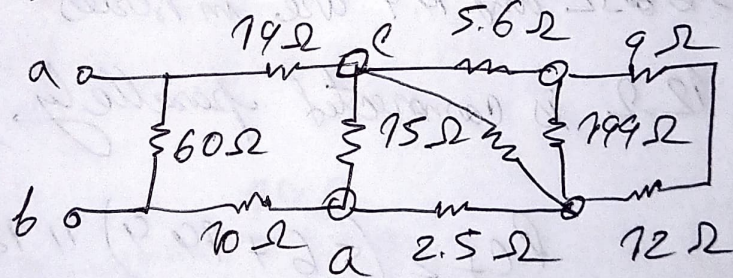


Here,  $2.5\Omega$  with an short circuit wire  $2.5\Omega$  is not useable

The circle,



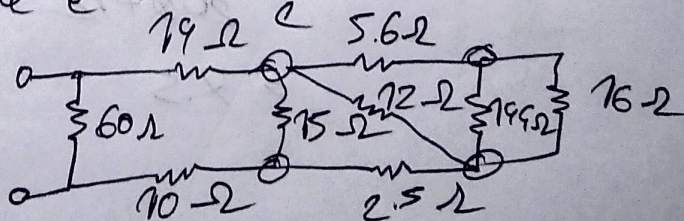Since,  $4\Omega$  and  $12\Omega$  is connected in series between node e and f






76  $\Omega$  and 144 is connected by parallelly

$$R_{eq} = \left( \frac{76 \times 144}{76 + 144} \right) \Omega$$

$$= 79.9 \Omega$$

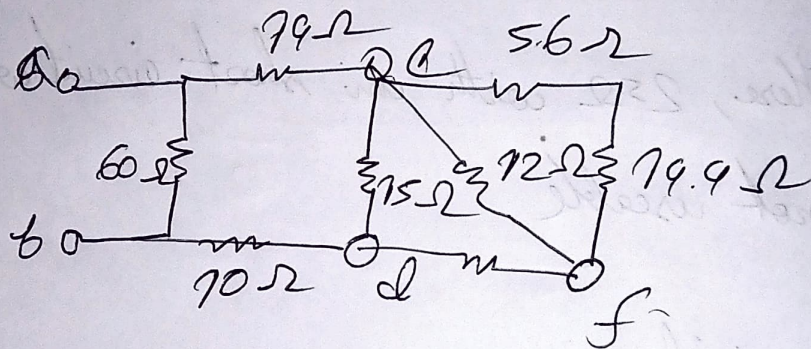

5.6  $\Omega$  and 79.9 are in series

12  $\Omega$  is connected parallelly,


$$R_{cf} = (5.6 + 79.9) \parallel 12 \Omega$$

$$= 20 \Omega \parallel 12$$


$$= \frac{20 \times 12}{20 + 12} \Omega$$

$$= 7.5$$



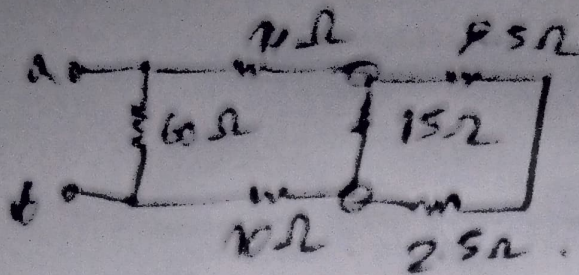


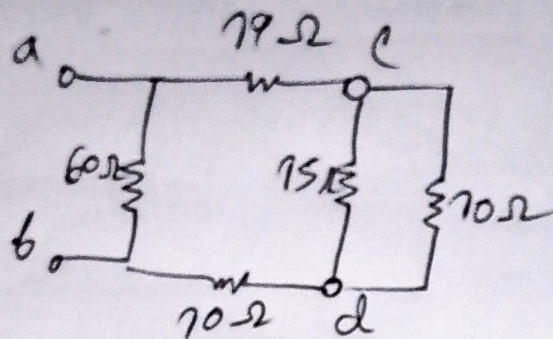$75\Omega$  and  $25$  connected in series .



$15\Omega$  and  $10\Omega$  are parallel
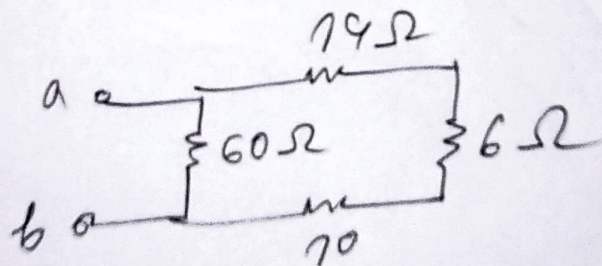
$$R_{cd} = \frac{15 \times 10}{15 + 10} = 6\Omega$$



$$R_{ab} = 60 \parallel (100 + 10 + 6)\Omega$$

$$= 60 \parallel 116\Omega$$

$$= \frac{60 \times 116}{60 + 116}\Omega$$

$$= 20\Omega \quad [\text{Ans}]$$